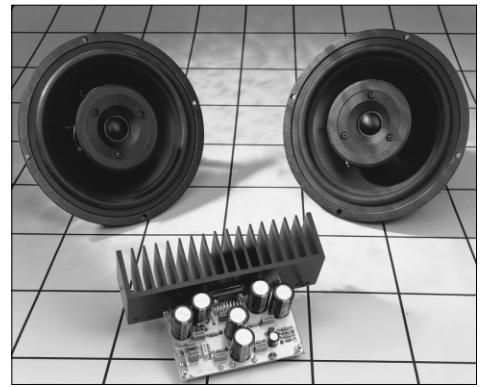


30 W AF AMPLIFIER FOR CARS

Design by T. Giesberts

The power that can be obtained from a standard car radio amplifier operating from a 12 V car battery is 5–6 W, which (for many listeners) is not really enough for satisfactory hi-fi reproduction. It is, of course, possible to boost the 12 V supply with a power inverter, but that is fairly expensive and not always acceptable. Now, a Philips IC enables audio power of about 30 W to be obtained from a 12 V car battery.



Until not so long ago, the Class B output stages of a standard car radio could not deliver more than $2 \times 5\text{--}6\text{ W}_{\text{rms}}$ into $4\ \Omega$ loudspeakers. More was not possible with a single supply line of 12 V. Most modern car radios use bridge amplifiers to boost the output to 12–16 W. Often, each of the four loudspeakers has its own dedicated amplifier. Many car manufacturers do not like the use of power inverters to raise the on-board voltage out of fear that these can cause (embarrassing or even dangerous) interference with the remainder of the electronic systems in the car (of which there can be many). There is also the problem of heat generation in the output stages, which may necessitate forced cooling.

Class H

Electronics manufacturers have been researching ways and means of obtaining adequate output power without the use of a power inverter, and Philips have come up with the TDA1560Q.

Output amplifiers can be arranged in a number of different configurations, of which most audio enthusiasts only know Class A and Class B. A different one that provides fairly high output power with relatively low dissipation is Class G. In this configuration, use is made of two supply voltages: a fairly low one that is constantly available and a much higher one that becomes available only when the the voltage swing of the output stages can not be sustained by the low supply voltage.

Since in cars only one supply voltage is available, Philips engineers have devised a pseudo Class G configuration in which a number of electrolytic capacitors are charged by the battery voltage. During brief voltage peaks in the output signal, semiconductor switches connect these capacitors in series with the 12 V line so that the supply voltage to the amplifier is temporarily doubled. Since this is a further de-

velopment of the Class G technique, it is named Class H. The (temporary) 24 V supply to the amplifier enables (theoretically) a power of 80 W to be delivered into $4\ \Omega$ or 40 W into $8\ \Omega$.

A simplified diagram of a Class H output amplifier is shown in Fig. 1. It contains two principal circuits: the first is a Class B amplifier, $T_1\text{--}T_4$, which is loaded by R_1 , and the second raises the internal

Brief Technical Data

Class H operation	
Low dissipation with music signals	
Extensive protection circuits (output current; temperature; load impedance)	
Supply voltage	12 V nominal
Quiescent current	100 mA
Output power	
(1 kHz sinusoidal, THD = 0.5%)	30 W r.m.s. into $8\ \Omega$
(music signal)	40 W into $8\ \Omega$
THD + noise (1 W into $8\ \Omega$)	<< 0.01% (1 kHz)
	<< 0.05% (20 Hz to 20 kHz)
THD + noise (20 W into $8\ \Omega$)	<< 0.06% (1 kHz)
	<< 0.2% (20 Hz to 20 kHz)
Power bandwidth (-3 dB)	5 Hz to 100 kHz

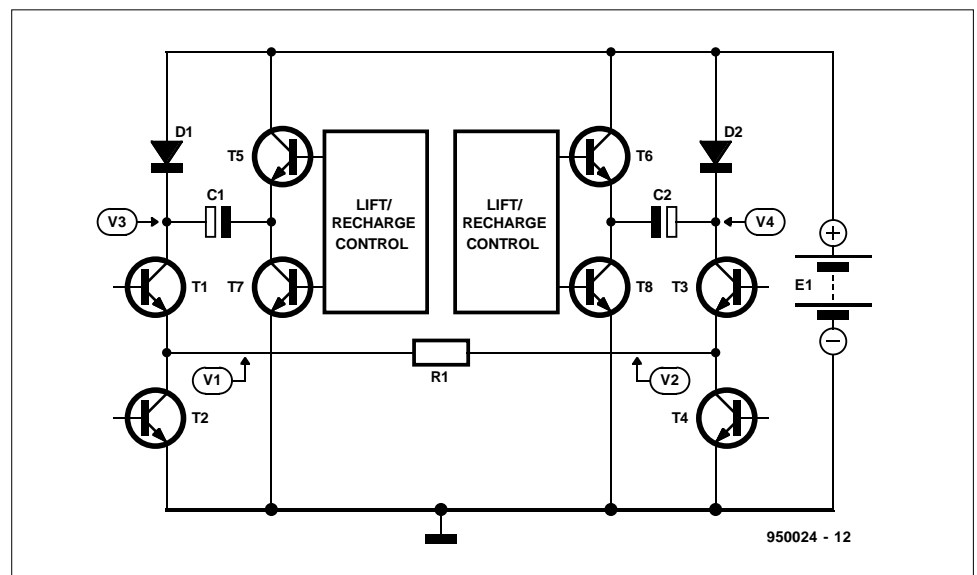


Fig. 1. Diagram of a basic Class H amplifier.

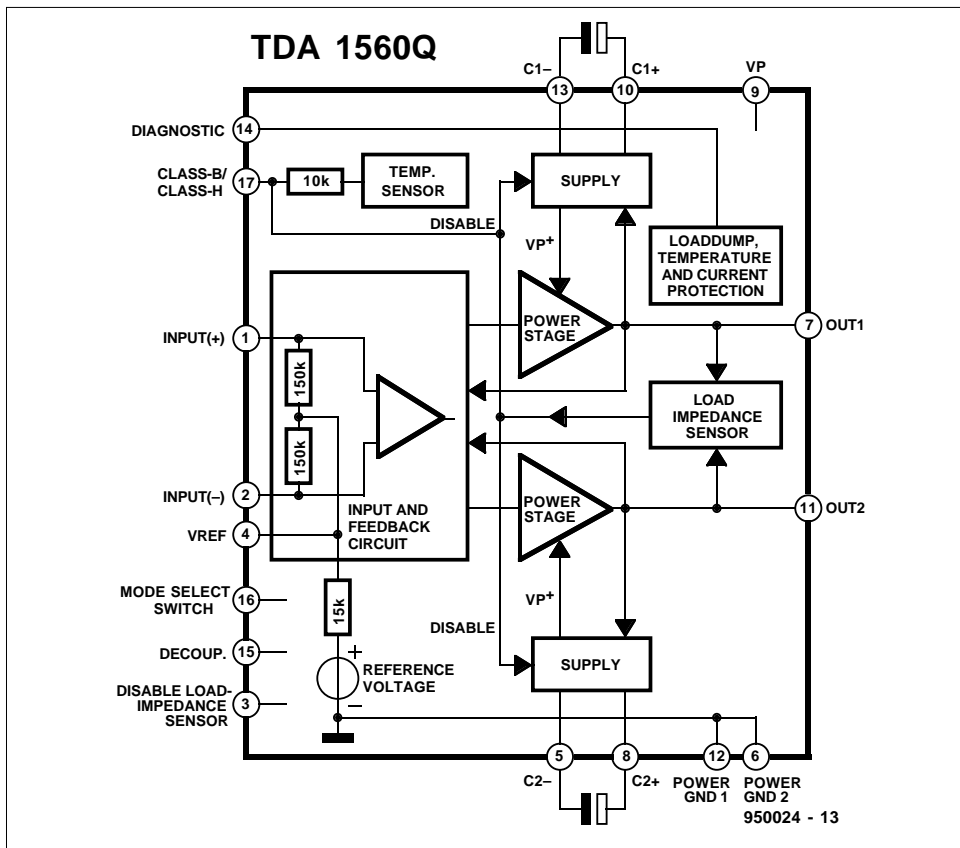


Fig. 2. Block diagram of the TDA1560Q

supply voltage. The second circuit uses two external capacitors, C_1 and C_2 , which serve as supply buffers.

Since a music signal consists only for a small part of high level components, the

supply voltage needs to be raised for a small part of the time only.

Because the supply voltage is raised for short periods of time only, the average dissipated power will be only slightly higher

than that of an amplifier without a voltage-raising circuit, in spite of the fact that the peak output power is appreciably higher.

Capacitors C_1 and C_2 are charged through current sources T_7 and T_8 to a voltage which is nearly equal to the supply voltage, E_1 . When either voltage V_1 (or V_2) rises and T_1 (or T_3) approaches the saturation voltage, the lift control circuit detects this. Lift transistors T_5 and T_6 then conduct, so that the charged capacitors are switched between the collector of T_1 (or T_3) and supply voltage E_1 . Diodes D_1 and D_2 prevent the capacitors being discharged via the battery. Voltage V_1 (or V_2) can increase to nearly twice the supply voltage. The lift/recharge control circuit ensures that T_5 and T_7 , and T_6 and T_8 , can not conduct simultaneously.

Inside the TDA1560Q

A block diagram of the TDA1560Q is shown in Fig. 2. A differential input stage in the input and feedback circuit is connected to pins 1 and 2. Because of this stage, the IC is highly insensitive to common-mode interference. The input impedance is 300 k Ω , so that for a good low-frequency response even small input capacitors are sufficient.

The input and feedback circuit contains circuitry that controls the supply circuits and the power stages.

The control circuitry monitors the input signal and anticipates saturation of the output transistors. As soon as this happens, the supply voltage is raised. Because the input signal is monitored, it is possible to

$R_1 = 390 \Omega$
 $R_2 = 150 \text{ k}\Omega$
 $R_3 = 8.2 \text{ k}\Omega$
 $R_4 = 1 \text{ M}\Omega$
 $R_5 = 10 \text{ k}\Omega$
 $R_6\text{--}R_9 = 2.2 \Omega$

Capacitors:

$C_1, C_2 = 1 \mu\text{F}$, pitch 5 mm
 $C_3 = 3.9 \text{ nF}$
 $C_4 = 10 \mu\text{F}$, 63 V, radial
 $C_5 = 220 \text{ nF}$, 35 V, tantalum
 $C_6\text{--}C_9, C_{17} = 220 \text{ nF}$
 $C_{10} = 22 \mu\text{F}$, 40 V, radial
 $C_{11}\text{--}C_{16} = 4700 \mu\text{F}$, 16 V, radial

Semiconductors:

$D_1 = \text{zener}$, 3.3 V, 500 mW
 $T_1 = \text{BC516}$

Integrated circuits:

$\text{IC}_1 = \text{TDA1560Q}$

Miscellaneous:

Heat sink for IC_1 ; $R_{\text{th}} \ll 2.5 \text{ K W}^{-1}$
 PCB Order No. 950024-1

[950024]

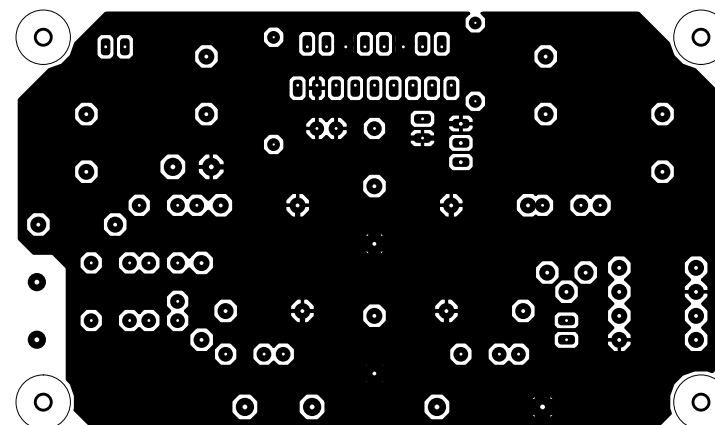
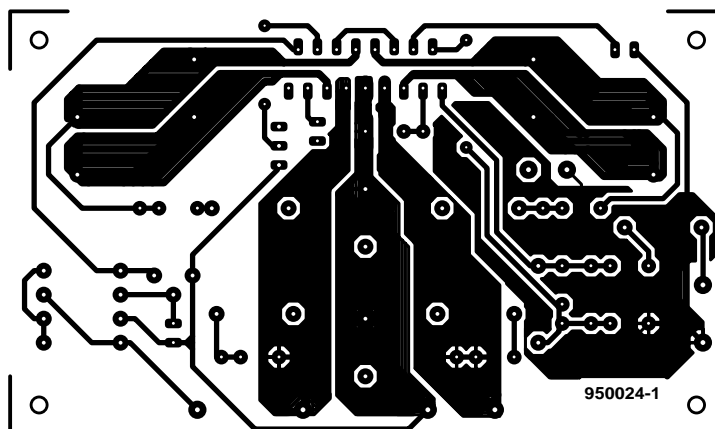
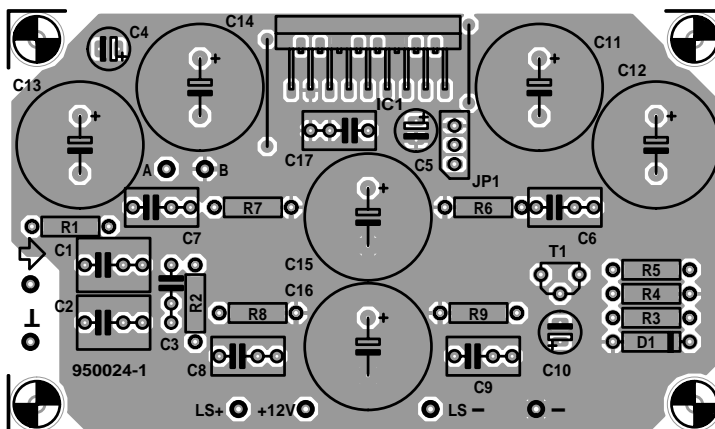


Fig. 4. Printed circuit board for the 30 W AF amplifier for cars.

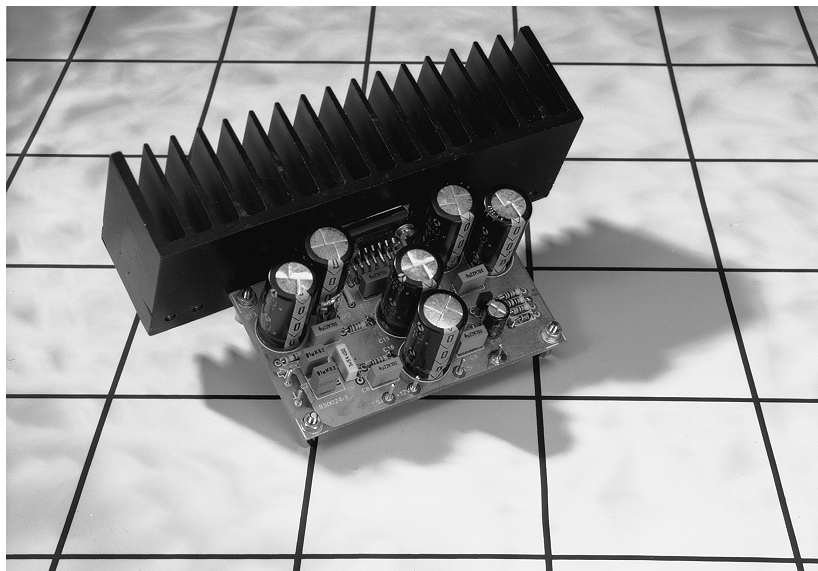


Fig. 5. The completed (prototype) 30 W AF amplifier for cars.