
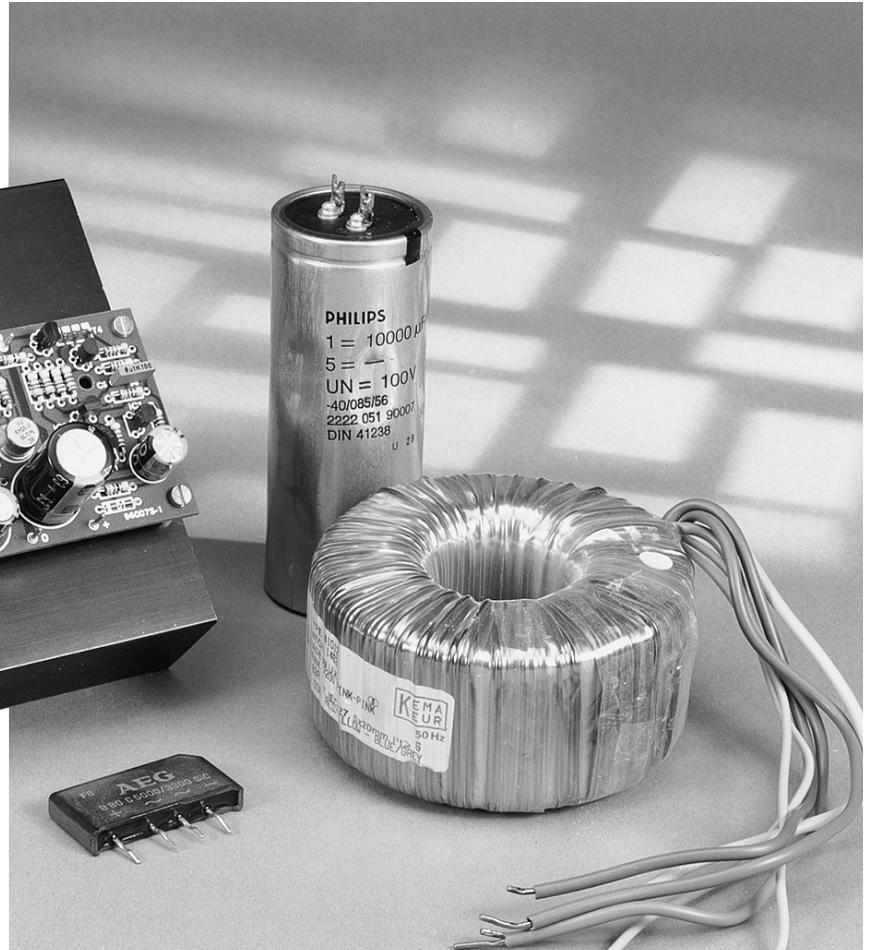

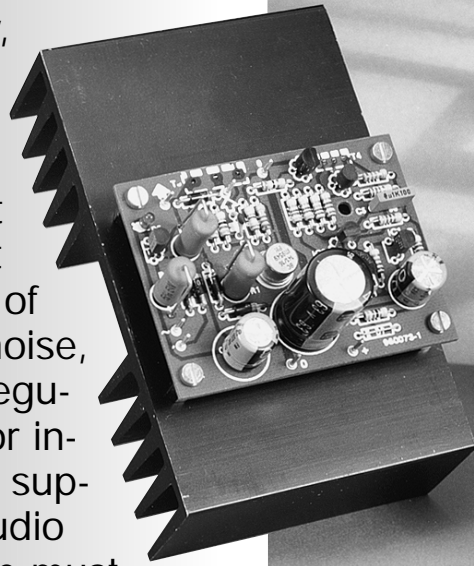
# active power buffer

Frequently, a direct voltage is required in a circuit that must be free of hum and noise, but not regulated. For instance, the supply to an audio output stage must be able to vary with the mains voltage and the load. Another example is when in the workshop a variable-ratio transformer (variac) is to produce a well-filtered direct voltage with good loading capacity for general purposes.



---

## *with temperature monitor*

---

The hum emanating from an unregulated power supply is normally caused by too high a current drain or too small a reservoir capacitor. Enlarging the capacitor is often the simplest, but not always the most effective, way of dealing with the problem. Hum is the manifestation of a ripple on the output voltage and it is best to suppress this in an active manner.

The circuit diagram in **Figure 1** looks like that of a conventional series regulator, but has no regulating amplifier with control comparator. Therefore, the output voltage automatically adapts itself in accordance with the

input alternating voltage and the current through the load. Consequently, the entire hum voltage is applied to the collector-emitter junction of darlington transistor  $T_3$ . The advantage of such an arrangement lies in a drastic reduction of the maximum dissipated power (at the highest mains voltage).

The lower part of the figure is a temperature monitor in which  $T_4$  is the sensor. If this transistor detects an over-temperature, the monitor circuit pulls the base of driver  $T_2$ , and thus that of  $T_3$ , to ground. This effectively cuts off the output current, so that no more power is dissipated.

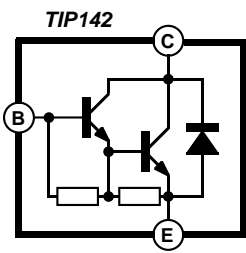
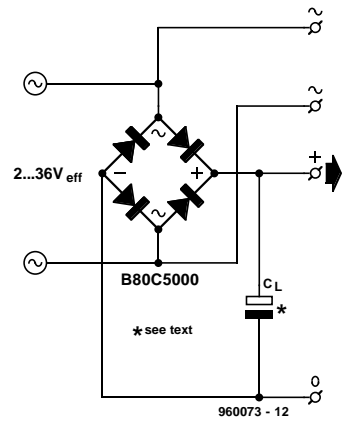
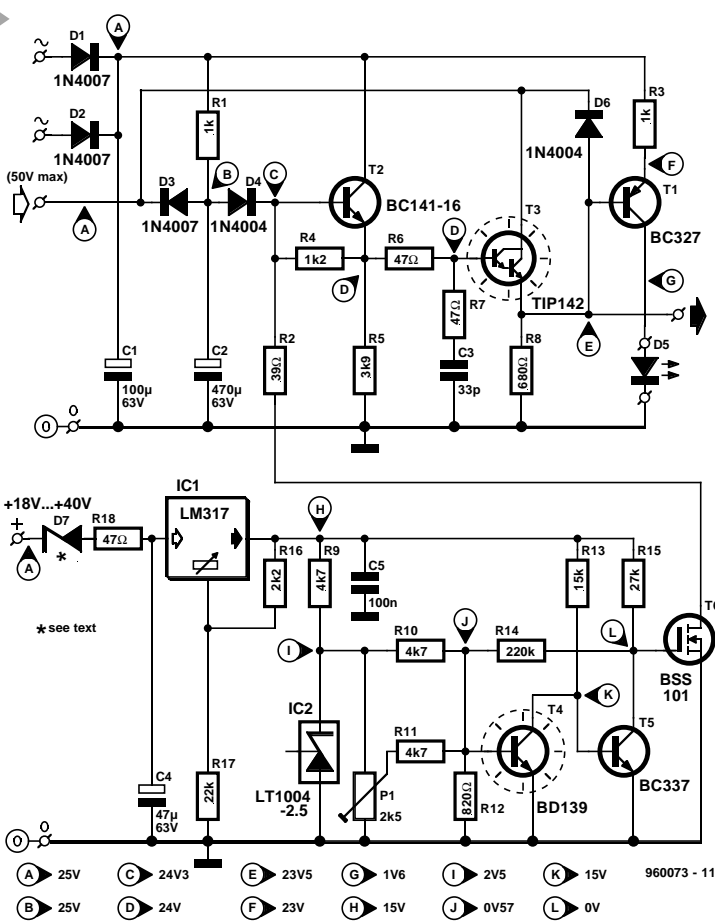


Figure 1. Circuit diagram of the active power buffer, including temperature monitor.

**CIRCUIT DESCRIPTION**

The circuit is arranged so that the power section (upper part of the figure) and the temperature monitor have their own rectifier. That for the monitor is the bridge rectifier, shunted by reservoir capacitor  $C_L$ , while  $D_1$  and  $D_2$  serve the power section.

Whereas the potential across  $C_L$  has a ripple whose level depends on the load current, the voltages across  $C_1$  and  $C_2$  are virtually free of ripple, since the load is small. The potential across  $C_1$  is about equal to the peak value of the alternating voltage applied to the bridge rectifier. The voltage across  $C_2$  depends on the minimum level across  $C_L$ ,  $U_{o(min)}$ , because it is pulled down by  $D_3$  twice in each mains period to  $U_{o(min)} + U_{D3}$ . The potential across  $C_2$ ,  $U_{C2}$ , determines the output voltage, which is about  $U_{C2} - 4U_{D3}$ .

Diode  $D_4$  is necessary to ensure that  $U_{CE}$  of emitter follower  $T_2$  retains a nominal value when the potential across  $C_1$  is a minimum. Resistors  $R_4$  and  $R_5$  ensure that the direct current through  $T_4$  is not too dependent on the current amplification of the transistor and the load current.

Resistor  $R_1$  provides the charging current for  $C_2$ , which must, of course, always be greater than the current

through  $D_4$  and the base current of  $T_2$ . Since the drop across  $R_1$  increases the dissipation of  $T_3$ , the resistor should be kept as small as possible. It should be not too small, however, because at large load currents it determines the ripple on  $U_{C2}$ . Its specified value is a compromise between these conflicting requirements.


Since the base of  $T_3$  is fed from the inductive output of  $T_2$ , resistor  $R_6$  is necessary to obviate any tendency of the darlington to oscillate. Note that  $R_7$  and  $C_3$  already tend to make the reactance more resistive.


Resistor  $R_8$  provides a minimum load for the circuit.

Resistor  $R_5$  prevents driver  $T_2$  from switching off during the quiescent state when  $T_3$  draws only a tiny base current.

Transistor  $T_1$  draws a current through  $D_5$ , which is more or less directly proportional to the peak hum voltage and inversely proportional to the value of  $R_3$ . This means that the

Figure 2. A 100 Hz hum voltage and the direct voltage at the output that depends on the load current; input alternating voltage is 20.7 V.

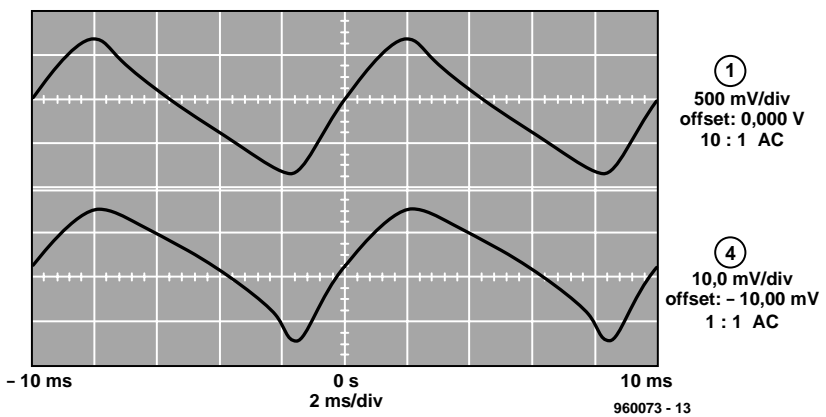

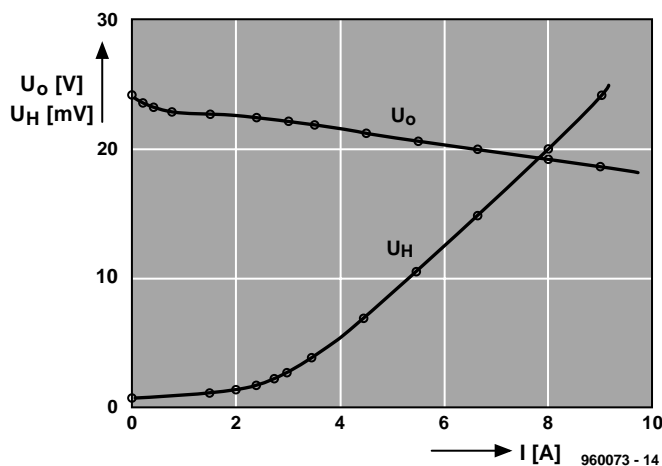

**Figure 3.** Hum voltage vs time at the input and at the output of the circuit.

brightness of the LED increases with rising load current.

Diode  $D_6$  comes into action only when, for instance, the circuit is being used to charge a battery and the mains fails. The diode then prevents too high a reverse-bias voltage at the base-emitter junctions of  $T_2$  and  $T_3$ .

The output resistance,  $R_o$ , of the circuit depends in the first instance on the value of  $C_L$  and the peak-to-peak value of the hum voltage,  $U_{H(pp)}$ , across this capacitor:

$$R_o \approx U_{H(pp)} / I_o \approx 1/2 f C_L,$$

where  $f$  is the mains frequency. Thus, if  $C_L = 10 \text{ mF}$ ,  $R_o = 1 \Omega$ .

The residual hum voltage at the output depends on load current  $I_o$ . This is shown diagrammatically in **Figure 2**, which assumes an output voltage of 24 V. When the load current is 10 A, hum suppression is about 30 dB. Note that the frequency of  $U_H$  is 100 Hz. **Figure 2** also shows the relationship between  $U_o$  and  $I_o$ . From this it will be seen that  $R_o = 0.3 \Omega$ .

These measurements were carried out with the input alternating voltage held constant at 20.7 V. In practice, this voltage drops somewhat owing to the internal resistance of the transformer.

**Figure 3** shows the hum voltage at the input and output. Note that the hum suppression at peak-to-peak values is about 50, that is, 34 dB, or a little better than previously.

If the average direct voltage at  $T_3$  is made equal to half the hum voltage, the dissipated power,  $P$ , is

$$P = U_a \cdot I_o = I_o^2 / 4fC_L.$$

Thus, when  $I_o = 10 \text{ A}$  and  $C_L = 10 \text{ mF}$ , the power dissipation is 50 W. Note that this value is independent of the output voltage.

## TEMPERATURE MONITOR

For input voltages greater than about 6 V, the circuit is not proof against sustained short-circuits.

It has, however, a temperature monitor which arranges for the load to be disconnected when the temperature rises above a preset level. This arrangement is particularly sensible for occasions when, for instance, the present circuit is used in conjunction with a variac for various purposes when an unwanted overload can happen all too easily.

The sensor is a Type BD139 transistor, which should be mounted on a suitable heat sink. The sensor action is effected by the temperature dependence of the base-emitter voltage, which is easily computed. The sensor and  $T_5$  form a Schmitt trigger with temperature-dependent threshold and hysteresis.

The base-emitter voltage of  $T_4$  is held constant by  $IC_2$  at a value set with  $P_1$ , at which the monitor comes into action when the temperature of the heat sink reaches 85–90 °C. When that happens,  $T_6$  pulls the base of  $T_2$  to ground via  $R_2$ , whereupon  $T_3$  is cut off and the output is open-circuited.

Power for the monitor circuit is derived from a mains adaptor that must provide at least 18 V. It may also be taken from the + terminal of  $C_L$  if the potential across this capacitor lies between 18 V and 40 V. If it is higher than 40 V, it is pulled to this value by  $D_7$ . The rating of this zener diode must be such that the voltage at the input of  $IC_1$  remains below 40 V when  $U_{CL}$  is a maximum and above 18 V when  $U_{CL}$  is a minimum.

## CONSTRUCTION

The circuit complete with temperature monitor is best built on the printed-circuit board shown in **Figure 4** (which unfortunately is not available ready made). The two sections of the circuit

are linked on the board by the common earth track at the centre and the connection from  $T_6$  to the base of  $T_2$  via  $R_2$ . If this resistor is omitted, the two sections are completely isolated from one another (apart from the common earth track).

If  $D_7$  is not used, it should be replaced by a wire bridge.

Note that  $T_3$  and  $T_4$  are fitted at the track side of the board. When the board is fitted on to the heat sink as in **Figure 5**, these transistors must be fitted on to the heat sink with the aid of insulating washers, screws and nuts. Two holes are provided in the board near  $T_2$  and  $T_5$  to allow access to the relevant screws.

Connect the ~ terminals from the bridge rectifier to the relevant terminals on the board via light-duty insulated circuit wire, and the + and 0 terminals to the relevant terminals on the board by medium-duty insulated circuit wire.

The buffered output is available at the emitter terminal of  $T_3$ .

## INITIAL TEST

The circuit may be tested by checking whether the voltages measured at various points indicated in **Figure 1** coincide with the values shown in that figure. The values were measured in the prototype with an input voltage of 25 V and an open-circuit output.

## SETTING UP

The temperature at which the monitor switches off the output is set with  $P_1$ . This temperature is determined by the heat resistance of the heat sink on which  $T_3$  is fitted. If this is  $1.8 \text{ K W}^{-1}$ , for instance, and the output power is 40 W, the temperature of the heat sink is  $1.8 \times 40 = 72 \text{ K}$  with respect to the ambient temperature. The temperature of the power transistor itself is another 40 K above this, so that, when the ambient temperature is 25 °C, it reaches 137 °C. The maximum permissible temperature of the TIP142 is 150 °C.

Set  $P_1$  fully anticlockwise and load the circuit with a power resistor of  $0.5 \Omega$ , rated at  $\geq 32 \text{ W}$  and set the input voltage derived from a variac to such a value that the output current is 8 A (maximum current through the TIP142 is 10 A). If only a fixed alternating voltage is available as input, the load resistance should be chosen to cause a current of about 8 A to flow through it. The voltage at the power transistor depends on the value of  $C_L$ , and it is well known that the tolerances of electrolytic capacitors vary widely. Therefore, it is better to measure the collector-emitter voltage and multiply this by the current to arrive at the dissipated power, which should be about 40 W. At this power, the LED should light.

## Parts list

### Resistors:

$R_1, R_3 = 1 \text{ k}\Omega, 5 \text{ W}$   
 $R_2 = 39 \Omega$   
 $R_4 = 1.2 \text{ k}\Omega$   
 $R_5 = 3.9 \text{ k}\Omega$   
 $R_6, R_7, R_{18} = 47 \Omega$   
 $R_8 = 680 \Omega, 5 \text{ W}$   
 $R_9-R_{11} = 4.7 \text{ k}\Omega$   
 $R_{12} = 820 \Omega$   
 $R_{13} = 15 \text{ k}\Omega$   
 $R_{14} = 220 \text{ k}\Omega$   
 $R_{15} = 27 \text{ k}\Omega$   
 $R_{16} = 2.2 \text{ k}\Omega$   
 $R_{17} = 22 \text{ k}\Omega$   
 $P_1 = 2.5 \text{ k}\Omega \text{ preset}$

### Capacitors:

$C_1 = 100 \mu\text{F}, 63 \text{ V}, \text{ upright}$   
 $C_2 = 470 \mu\text{F}, 63 \text{ V}, \text{ upright}$   
 $C_3 = 33 \text{ pF}$   
 $C_4 = 47 \mu\text{F}, 63 \text{ V}, \text{ upright}$   
 $C_5 = 100 \text{ nF}$

### Semiconductors:

$D_1-D_3 = 1\text{N}4007$   
 $D_4, D_6 = 1\text{N}4004$   
 $D_5 = \text{LED}, \text{ high-efficiency, red}$   
 $D_7 = \text{see text}$   
 $T_1 = \text{BC}327$   
 $T_2 = \text{BC}141-16$   
 $T_3 = \text{TIP}142$   
 $T_4 = \text{BD}139$   
 $T_5 = \text{BC}337$   
 $T_6 = \text{BSS}101 \text{ (Siemens)}$

### Integrated circuits:

$\text{IC}_1 = \text{LM}317\text{LZ}$  (National Semiconductor)  
 $\text{IC}_2 = \text{LT}1004-2.5$  (Linear Technology) or  $\text{LM}336-2.5$  (National Semiconductor)

### Miscellaneous:

Heat sink  $1.8 \text{ K W}^{-1}$   
 Insulating washers, screws and nuts for  $T_3$  and  $T_4$

Wait about 30 minutes, after which the heat sink temperature should be about 72 K higher than the ambient temperature (as computed earlier). It is, of course, better to measure the temperature, but this presupposes that a suitable thermometer is available.


When the stated temperature has been reached, turn the wiper of  $P_1$  carefully clockwise until the LED lights brightest. The monitor then comes into action: the current is cut off and the temperature drops.

Wait a while for the temperature to reach a lower value, when the monitor should be deactivated, and an output current flows again.

Increase the power dissipation slightly and repeat the foregoing. In this way, average cut-off and switch-on temperatures will be set.


[960073]

4

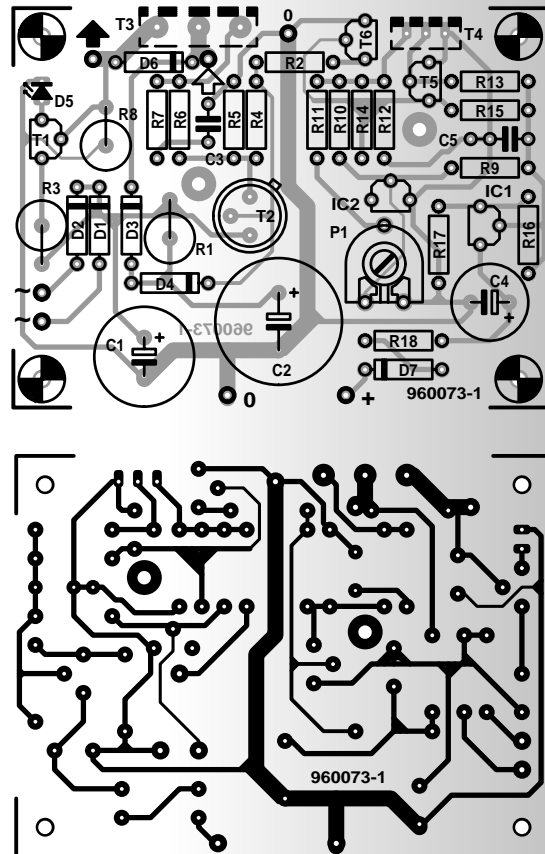

**Figure 4.** The printed-circuit board for the active power buffer, including temperature monitor.

5

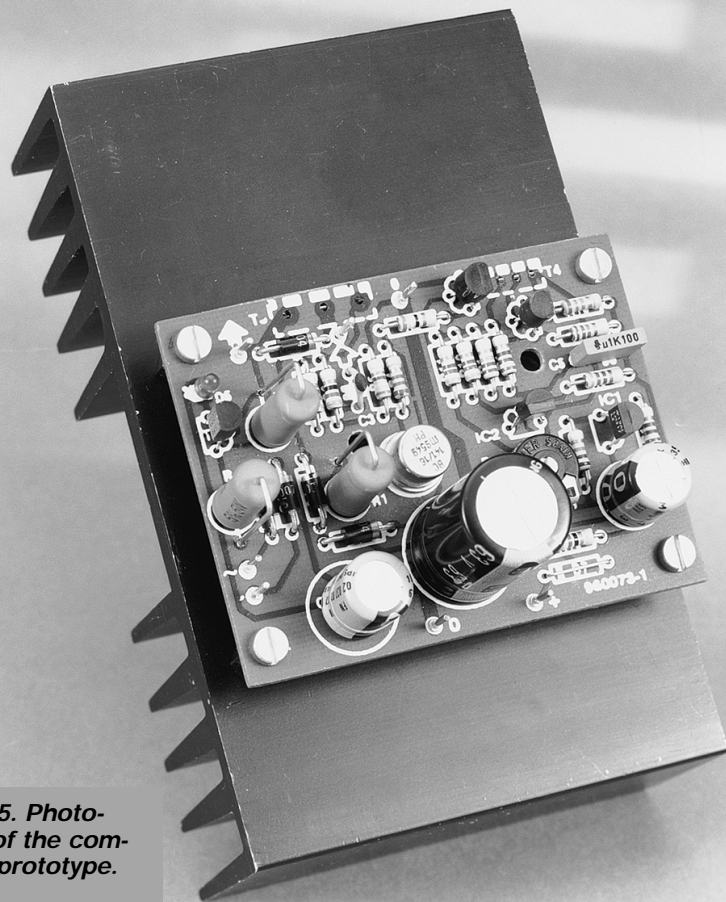

**Figure 5.** Photograph of the completed prototype.