



# sampling rate converter

Although there are still dyed-in-the-wool sound technicians who swear by the good old analogue recording technology, most others, bitten by the digital audio recording bug, do not want to revert to analogue recording. They have experienced the pleasures of loss-free processing and copying of recordings at digital level. These pleasures turn to frustration, however, when they want to convert a DAT recording on to a CD. This cannot be done just like that because the two have different sampling frequencies: DAT 48 kHz, and CD 44.1 kHz. To overcome this difficulty, a converter as described in this article is required.



It is a regrettable fact, with which we will have to learn to live, that different audio techniques use incongruous sampling frequencies (CDI – 18.9 kHz; 8 mm VCR – 31.5 kHz; NICAM – 32 kHz; CDI – 37.8 kHz; VCR – 44.056 kHz; CD – 44.1 kHz; DAT – 48 kHz; and others).

The growing popularity of digital audio is creating an increasing need of some means of coupling equipment using such different techniques – without loss of quality, of course. This can be done by altering the sampling rate in one of the two units to be coupled, while ensuring that the two sampled signals are adequately synchronized. Clearly, this requires a well-designed intelligent converter.

The design of the present converter is based on a dedicated IC: the Type TDA1373H from Philips. This circuit is very versatile and may be used for almost any imaginable conversion (but not quite – see later). Thus, it can be used for converting a DAT recording into a CD recording. Also, it enables CD data to be recorded on a DAT machine with a sampling rate of only 32 kHz, which, of course, results in a much longer playing time. Another possibility is converting the consumer standard s/PDIF\* to the professional AES/EBU\*

format. True, the converter has no AES/EBU connectors, but the conversion is possible.

Apart from as a converter, the circuit may be used as a copybit eliminator. In that case, the two sampling rates are made equal (as in the converter), but the category code, the copybit and the generation-status bit are set. The sampling rate used must correspond with the code set in most DAT machines to ensure that the signal is accepted.


Finally, the circuit may also serve as jitter killer since the first-in-first-out (FIFO) and gain stage in the TDA1373H suppresses any jitter.

## DESIGN

The circuit of the converter is shown in the diagram of **Figure 1**. Circuit IC<sub>1</sub> is the integrated digital converter, IC<sub>2</sub> is the controller, and IC<sub>3</sub> is the output interface.

The most important property of the TDA373H is the integrated Audio Digital Input Circuit (ADIC), which enables the chip to decode IEC958 signals (S/PDIF or AES/EBU). The circuit can work on a stand-alone basis or be controlled by a microprocessor. In the present circuit, it is controlled by IC<sub>2</sub>, since this gives a wider choice of output formats. The circuit can process up to 20 bits and afterwards provides the con-

Design by T. Giesberts

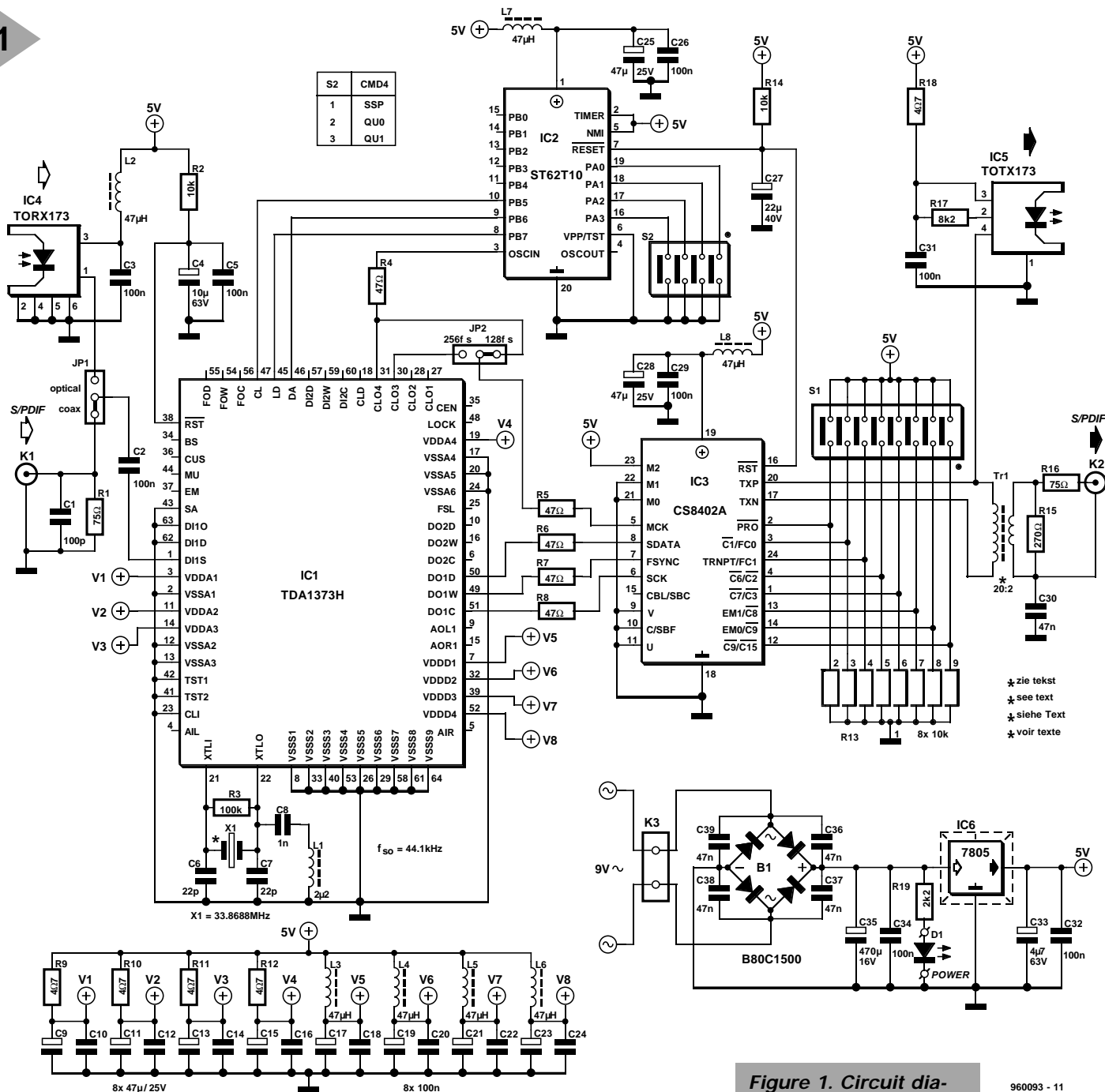

**Figure 1. Circuit diagram of the sampling rate converter in which IC<sub>1</sub> is the actual converter, IC<sub>2</sub> is the controller, and IC<sub>3</sub> is the output interface.**

960093 - 11

verted data in 16-, 18-, or 20-bit format.

The TDA373H is designed to provide up to four different applications, but since the present circuit is geared to being used as a sampling rate converter, the circuit is limited to this application.


The input of the converter may be optical (via IC<sub>4</sub>) or coaxial (via K<sub>1</sub>). The selection between these two is

by jumper JP<sub>1</sub>, since it is assumed that the converter will be used invariably in a fixed setup in which there is seldom or never a need for changing from one to the other. The remaining two input pins of IC<sub>1</sub> are linked to earth.

Correct operation of IC<sub>1</sub> requires the setting of six command registers, which is effected by controller IC<sub>2</sub>.

After a brief power-up reset (by R<sub>14</sub>-C<sub>27</sub>), IC<sub>2</sub> sends twelve 8-bit words (six addresses and data) to IC<sub>1</sub> via a serial connection.

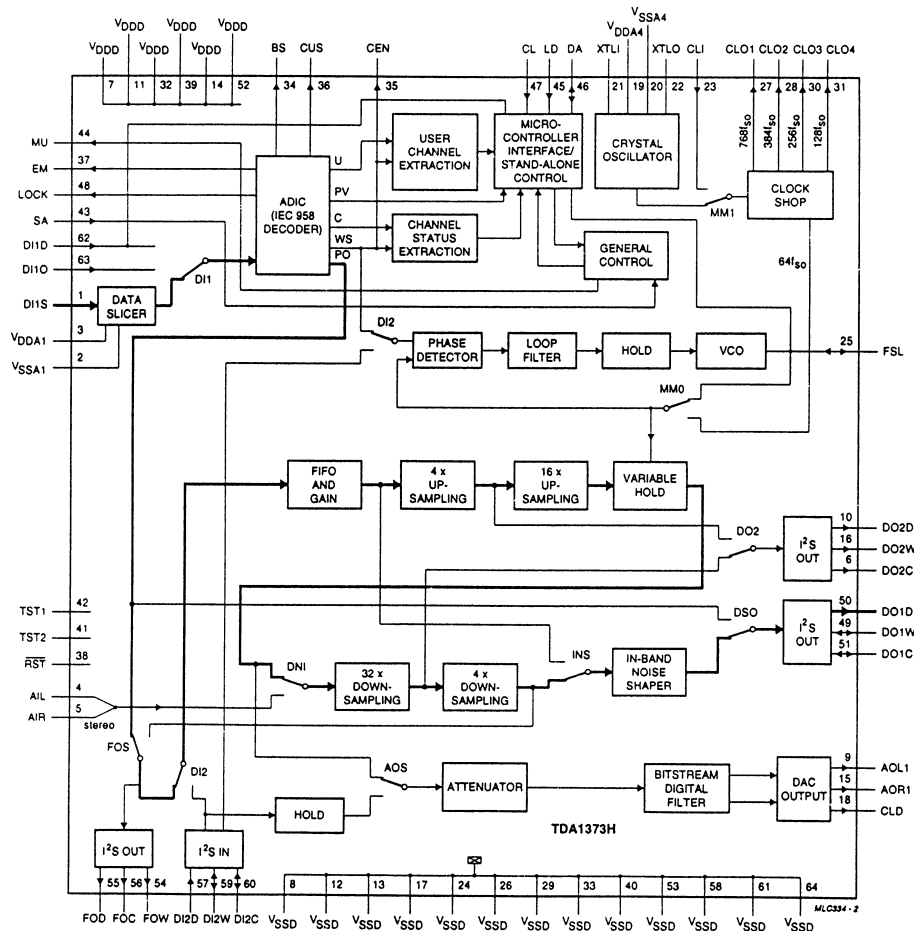The in-band noise shaper and the stop-band suppression of the ×64



960093 - 12

**Figure 2. IC<sub>1</sub> affords various functions. The relevant signal paths for the sampling rate conversion are indicated by bold lines.**

oversampling filter are set by, respectively, sections 2, 3 and 1 of quadruple DIP switch S<sub>2</sub>. The switches are debounced by a delay of 1-1½ seconds between their being operated and the relevant function being actuated. This delay is effected by the controller.

The sampling rate of the output signal, f<sub>s(o)</sub>, of IC<sub>1</sub> is determined by the crystal between pins 21 and 22, according to equation

$$f_{x1} = 768 f_{s(o)}$$

Thus, the crystal frequency should be 33.8688 MHz for a sampling rate of 44.1 kHz, and 24.576 MHz for a sampling rate of 32 kHz.

The sampling rate of the input, f<sub>s(i)</sub>, must be not lower than 0.35 f<sub>s(o)</sub>, nor higher than 1.45 f<sub>s(o)</sub>. Thus, if the circuit is used as IEC598 decoder only, the input sampling rate should not exceed 45 kHz if the output sampling rate is 32 kHz. If conversion from 48 kHz to 32 kHz is required, consideration should be given to using two converters in cascade.

The converted data are available at serial digital audio output 1 and applied to output interface IC<sub>3</sub> via resistors R<sub>6</sub>-R<sub>8</sub>, which provide di/dt limiting.

Circuit IC<sub>3</sub> is a digital audio in-

terface transmitter Type CS8402. This IC can also process various formats, but in the present circuit the serial input (pins, 6, 7 and 8) is fixed for I<sup>2</sup>S by the levels at inputs M0, M1 and M2. Virtually all functions of IC<sub>3</sub> may be obtained by appropriate setting of the various sections of DIP switch S<sub>1</sub>.

The symmetrical output at TXP, TXN. is converted into a standard S/PDIF output (0.5 V<sub>pp</sub> into 75 Ω). The electrical isolation provided by the transformer has the benefit of preventing earth loops.

An optical output is provided by optoisolator IC<sub>5</sub>.

The power supply may be based on a standard 9 V mains transformer or mains adaptor rated at not less than 300 mA. The supply lines are stabilized by regulator IC<sub>6</sub> and lavishly decoupled as shown in the diagram.

**THE TDA1373H**

The TDA1373H, called general digital input, is a circuit that provides four different modes of operation. However, the present application is that of sampling rate converter, SRC, and, therefore, only the parts relevant to this will be discussed in this section.

In the block diagram in Figure 2 the relevant signal paths are shown in bold lines.

The input signal is applied to the data slicer via pin DI1S. The slicer can handle signals at levels from 200 mV<sub>pp</sub> to 5 V<sub>pp</sub>.

The output of the slicer is applied to the audio digital input circuit, ADIC, which decodes the stereo audio samples, the word clock, the bit clock and various data (v, u, c and p) bits. The last function is not used here.

The ADIC locks to a 44.1 kHz signal in not more than 1 ms. Until it has locked, there is no word clock, and the audio bits are muted.

The output of the ADIC is applied to

**Table 1. Two different response curves of the x64 oversampling filter can be selected with section 1 of DIP switch S<sub>2</sub>.**

S2-1:				
bit SS	pass band		stop band	
0	0-0.45351f <sub>s(i)</sub>	±0.004 dB	0.54648-1f <sub>s(i)</sub>	-70 dB
1	0-0.46875f <sub>s(i)</sub>	±0.004 dB	0.53125-1f <sub>s(i)</sub>	-50 dB





# Test results

The quality and properties of the sampling rate converter were tested in the digital domain at the various output formats. The (analogue) generator of an Audio Precision Analyser was used as the digital signal source, and this was coupled to a 20-bit analogue-to-digital converter (ADC). Of the four characteristics shown, I represents the output spectrum of the ADC. The other three characteristics may be compared with this.

Note how well the action of the in-band noise shaper is seen in Characteristic IV; a clear rise is discernible only in the (virtually inaudible) range above 18 kHz.

At the same time, and with the same setup, the signal-to-noise ratio for the various output formats was determined:

  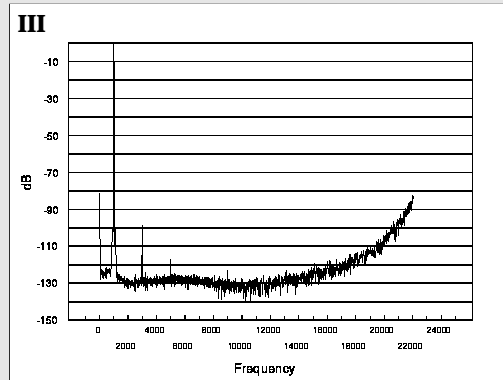 - 16 bit rounded off:  $-94.5$  dB;
- 16 bit INS:  $-89.7$  dB;
- 18 bit INS:  $-95.5$  dB;



- II: 16 bit rounded off (section 2 of  $S_2$  on; section 3 of  $S_2$  on).
- III: 16 bit INS (section 2 of  $S_2$  on; section 3 of  $S_2$  off).
- IV: 18 bit INS (section 2 of  $S_2$  off; section 3 of  $S_2$  off).

No characteristic is shown for the 20-bit mode (section 2 of  $S_2$  off; section 3 of  $S_2$  on), since, at least up to 20 kHz, this is all but identical to the input signal of the converter (Characteristic I).

- 20 bit:  $-97$  dB.

Note that the signal-to-distortion ratio of the ADC was 97.5 dB (measured without noise).

The signal-to-noise of the ADC plus sampling rate converter (without distortion) in the same test setup was about  $-107$  dB (dynamic range of the ADC). The dynamic range, measured at a digital-to-analogue converter, DAC, was about 5 dB better with 16 bit INS than with 16 bit rounded off.

the first-in-first-out, FIFO, and gain stage. The FIFO section equalizes any speed variations of the incoming samples. Its size is eight samples and it ensures a tracking speed of  $4 \text{ kHz ms}^{-1}$ .

The gain section enables the signal to be amplified or attenuated. In the present application, the signal is attenuated by 0.068 dB to prevent clipping in the digital filters.

The samples are fed for interpolation to a  $\times 64$  oversampling filter. This filter consists of a  $\times 4$  section and a  $\times 16$  section. There is a choice of two filter characteristics: one with


**Table 2. The word-length of the samples may be adapted with section 2 and 3 of DIP switch S<sub>2</sub>.**

S <sub>2</sub> -2:	S <sub>2</sub> -3:	
bit QU0	bit QU1	length of word
0	0	16 bit (rounded off)
1	0	20 bit
0	1	16 bit INS
1	1	18 bit INS

a stop-band suppression of 70 dB and the other with a stop-band suppression of 50 dB but with steeper skirts. The second is intended especially for use with signals with a sampling rate of 32 kHz, and a pass-band of 0–15 kHz as, for instance, in digital satellite radio. The characteristics are selected by section 1 of DIP switch S<sub>2</sub> – see also Table 1.

The samples are applied from the filter to the variable hold stage in which the actual sampling rate conver-

**Figure 3. IC<sub>3</sub> is a digital audio interface transmitter intended to encode and send audio data in accordance with the usual standards.**

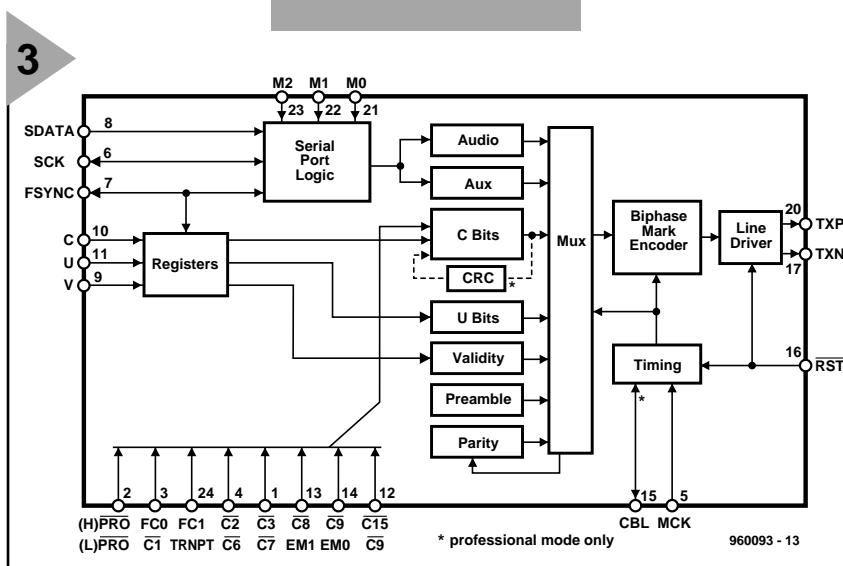

sion takes place. Depending on the ratio of the input sampling rate and the output sampling rate, the sample is used once or twice, whence the name variable hold. When the ratio is 1:1, all samples are used twice, since the down sampling is  $\times 128$ .

The variable hold function is controlled by a digital phase-locked loop, PLL, formed by the phase detector, loop filter, hold, and vco (voltage-controlled oscillator) stages.

The loop filter ensures that the PLL locks rapidly. This is necessary because, after power-up, the bandwidth of the filter is reduced in two steps from 500 Hz to 50 Hz and then from

50 Hz to 0.5 Hz. The frequency difference is only 1 Hz for 512 input samples (10 ms for a sampling rate of 44.1 kHz).

After the PLL has locked in, the audio signals are demuted and the conversion commences. To prevent any errors, the FIFO is monitored continuously in the variable-hold phase. As soon as the slightest tracking error is detected, the bandwidth of the loop filter is enlarged.

To convert the sampling rate to the requisite output value, the samples are passed through a  $\times 128$  down-sampling filter, which consists of a  $\times 32$  section and a  $\times 4$  section. The overall filter provides a stop-band suppression of 80 dB from 0.54648 of the output sampling rate.

Finally, the samples are applied to an in-band noise shaper, INS, which adapts the word-length of the samples to specific requirements. The standard

length of 20 bits may be reduced to 16 bits or 18 bits by the relevant sections of DIP switch S<sub>2</sub>. There are four possibilities as enumerated in Table 2, the first of

usual interface standards. The circuit provides the possibility of setting the most important channel status bits via seven inputs: pins 3, 24, 4, 1, 13, 14 and 12 in Figure 3. These inputs are controlled by octal DIP switch S<sub>1</sub> (see Figure 1). All seven inputs have a double function, which depends on the level at pin 2. This level is set with section 8 of S<sub>1</sub> and determines whether the IC works in the professional (AES/EBU) or in the consumer (S/PDIF) mode. The audio data are coded to the standard associated with the selected mode.

In the professional mode, a CRC code may be generated (channel status byte 23) as shown in dashed lines.

The serial input, pins 6, 7 and 8, can handle seven different formats and audio samples of 16–24 bits. In the present circuit, the format is fixed for I<sup>2</sup>S with M0, M1 and M2.

The serial inputs for channel status, c, user data, u, and validity, v, are not used and linked to earth. The v bit must be low to indicate that audio data are being processed which can be converted to analogue signals.

Pin 15, channel block start, CBL, is not used in the present application either. Normally, it is an output that may be used for writing c, u and v

**Table 3a. Sampling rates in professional mode.**

S <sub>1</sub> -8:	S <sub>1</sub> -5:	S <sub>1</sub> -4:	
PRO	C6	C7	
0	0	0	not defined
0	0	1	48 kHz
0	1	0	44.1 kHz
0	1	1	32 kHz

bits. CBL is an input only when in the professional mode the transparent option is chosen (in which the c, u and v bits can be looped in via a receiver). In this way, synchronization of signals coming from separate equipment is possible. Normally, the master clock, MCK, is  $128 f_s$ , where  $f_s$  is the signal frequency, but in the transparent mode,  $MCK = 256 f_s$ . The multiplier is set with jumper JP<sub>2</sub>.

**PROFESSIONAL MODE**

When pin 2,  $\overline{PRO}$ , is low, that is, when section 8 of S<sub>1</sub> is closed, the digital audio interface transmitter, IC<sub>3</sub>, is in the professional mode. In this mode, bits 1, 2, 3, 4, 6, 7 and 9 may be set after a 1 has been sent for channel status bit 0.

C0 indicates whether the channel status block applies to the professional (1) or the consumer (0) mode.

C1 determines whether the data are audio (0 – section 6 of S<sub>1</sub> closed) or

which is 20 bits.

The INS has a facility for adapting the digitization noise in a psycho-acoustical manner, whereby the noise to which human hearing is most sensitive is shifted upwards in frequency. This facility gives a subjective improvement of two bits with respect to the real quantization level.

Finally, the 20 bit length may be reduced to a 16-bit length by a simple rounding off action.

**CODING & CONTROL**

The digital audio interface transmitter, IC<sub>3</sub>, is intended primarily for coding and sending audio data according to

**Table 3b. Sampling rates in consumer mode.**

$S_{1-8}$ :	$S_{1-6}$ :	$S_{1-7}$ :	
PRO	FC1	FC0	
1	0	0	44.1 kHz
1	0	1	48 kHz
1	1	0	32 kHz
1	1	1	44.1 kHz, CD-mode

not audio (1 – section 6 of  $S_1$  open).

C2, C3 and C4 are coded by EM0 (section 2 of  $S_1$ ) and EM1 (section 3 of  $S_1$ ) and determine the emphasis to be used: for instance, 110 is 50/15  $\mu$ s.

C6 and C7 determine the sampling rate. The requisite setting of the rele-

**Table 4. Setting the category code.**

$S_{1-8}$ :	$S_{1-3}$ :	$S_{1-2}$ :	
PRO	C8	C9	
1	0	0	general format
1	0	1	PCM-en-coder/decoder
1	1	0	CD
1	1	1	DAT

vant sections of  $S_1$  is given in Table 3a.

A 1 at C9 (section 2 of  $S_1$  open) indicates a stereo signal; a 0 means that the mode is indeterminate.

In the transparent mode, none of the stated pins is used: the channel code is read at the c input only.

### CONSUMER MODE

When pin 2,  $\overline{\text{PRO}}$ , is high (section 8 of  $S_1$  open), the digital audio interface transmitter is in the s/PDIF (consumer) mode. In this mode, bits 2, 3, 8, 9, 15, 24 and 25 may be set after a 0 has been sent for channel status bit 0.

C0 – 0 – indicates that the channel status block applies to the consumer mode.

FC0 and FC1 determine the sampling rate. The requisite setting of the relevant sections of  $S_1$  is given in Table 3b.

C2 gives a choice between copy prohibit (0 – section 5 of  $S_1$  closed) or copy permit (1 – section 5 of  $S_1$  open).

C3 determines whether emphasis (50/15  $\mu$ s) will be applied (1 – section 4

of  $S_1$  open) or not (0 – section 4 of  $S_1$  closed).

C8 and C9 determine the category code: the requisite setting of the relevant sections of  $S_1$  is shown in Table 4.

C15 is the generation status bit. Depending on the category code, the function of this bit, determined by the setting of section 1 of  $S_1$ , is inverted. When the category code is 001xxxx, 0111xxx or 100xxxx, a 0 indicates that the bit is an original and a 1 that it is a copy. With all other category codes, the reverse is true.


When the copy bit is 1, there is no copy protection, so that copying is possible. If the copy bit is 0, the generation status bit, in combination with the category code, determines whether copying may be carried out or not.

The outputs of IC<sub>3</sub> are RS422 compatible line drivers that go low when the ic is being reset.

Make sure that the channel status bits are active low and that a 0 is set by closing the relevant section of the DIP switch.

### CONSTRUCTION

The converter is best built on the printed-circuit board shown in Figure 4. Although the board is compact, it affords ample space for all parts and components, including audio sockets K<sub>1</sub> and K<sub>2</sub> and optoisolators IC<sub>4</sub> and IC<sub>5</sub>. It does not have space for the mains transformer, however. Note that controller IC<sub>2</sub> is available ready programmed through our Readers services (see towards the end of this issue).

 

**Figure 4. Printed-circuit board for the sampling rate converter. Note that IC<sub>1</sub>, a surface-mount device, must be soldered at the track side.**

## PARTS LIST

### Resistors:

R<sub>1</sub>, R<sub>16</sub> = 75 Ω  
 R<sub>2</sub>, R<sub>14</sub> = 10 kΩ  
 R<sub>3</sub> = 100 kΩ  
 R<sub>4</sub>-R<sub>8</sub> = 47 Ω  
 R<sub>9</sub>-R<sub>12</sub>, R<sub>18</sub> = 4.7 Ω  
 R<sub>13</sub> = 8×10 kΩ array  
 R<sub>15</sub> = 270 Ω  
 R<sub>17</sub> = 8.2 kΩ  
 R<sub>19</sub> = 2.2 kΩ

### Capacitors:

C<sub>1</sub> = 100 pF  
 C<sub>2</sub>, C<sub>3</sub>, C<sub>5</sub>, C<sub>10</sub>, C<sub>12</sub>, C<sub>14</sub>, C<sub>16</sub>, C<sub>18</sub>, C<sub>20</sub>,  
 C<sub>22</sub>, C<sub>24</sub>, C<sub>26</sub>, C<sub>29</sub>, C<sub>31</sub>, C<sub>32</sub>, C<sub>34</sub> =  
 100 nF ceramic  
 C<sub>4</sub> = 10 μF, 63 V, radial  
 C<sub>6</sub>, C<sub>7</sub> = 22 pF

C<sub>8</sub> = 1 nF ceramic  
 C<sub>9</sub>, C<sub>11</sub>, C<sub>13</sub>, C<sub>15</sub>, C<sub>17</sub>, C<sub>19</sub>, C<sub>21</sub>, C<sub>23</sub>,  
 C<sub>25</sub>, C<sub>28</sub> = 47 μF, 25 V, radial  
 C<sub>27</sub> = 22 μF, 40 V, radial  
 C<sub>30</sub>, C<sub>36</sub>-C<sub>39</sub> = 47 nF, ceramic  
 C<sub>33</sub> = 4.7 μF, 63 V, radial  
 C<sub>35</sub> = 470 μF, 16 V, radial

### Inductors:

L<sub>1</sub> = 2.2 μH  
 L<sub>2</sub>-L<sub>8</sub> = 47 μH

### Semiconductors:

D<sub>1</sub> = LED, low current

### Integrated circuits:

IC<sub>1</sub> = TDA1373H (Philips)  
 IC<sub>2</sub> = ST6210 (see Readers services)  
 IC<sub>3</sub> = CS8402A (Crystal)  
 IC<sub>4</sub> = TORX173 (Toshiba)


IC<sub>5</sub> = TOTX173 (Toshiba)

IC<sub>6</sub> = 7805

### Miscellaneous:

JP<sub>1</sub>, JP<sub>2</sub> = 3-way pin header and jumper  
 K<sub>1</sub>, K<sub>2</sub> = audio socket for board mounting  
 K<sub>3</sub> = terminal block, pitch 5 mm  
 S<sub>1</sub> = octal DIP switch  
 S<sub>2</sub> = quadruple DIP switch  
 Tr<sub>1</sub> = wound on G2/3FT12 core - see text  
 B<sub>1</sub> = rectifier Type B80C1500  
 X<sub>1</sub> = see text  
 Heat sink for IC<sub>6</sub>: 29 k W<sup>-1</sup>, for instance, Fischer ICK35/SA, available from Dau, telephone 01243 553 031  
 PCB Order no. 960093 (see Readers services)  
 Mains transformer or mains adaptor, 9 V, 300 mA

5

 

**Figure 5. Top view of the completed prototype converter board.**

The completion of the board should not present any undue difficulties – see Figure 5 for a view of the top of a completed board.

Note that IC<sub>6</sub> is mounted on an appropriate heat sink.

Less experienced constructors may find the mounting of IC<sub>1</sub> and the construction of output transformer Tr<sub>1</sub> not so straightforward.

Circuit IC<sub>1</sub> is a surface-mount device, SMD, which should be soldered at the track side (underside) of the board using an iron with a very fine tip – see Figure 6. Note the correct way of fitting: pin 1 is identified by a small disk on the case: this side must point towards the connectors on the board.


Transformer Tr<sub>1</sub> is a DIY device which is wound on a G2/3FT12 core. The primary winding consists of 20 turns, and the secondary of two turns, of enamelled copper wire with a diameter of 0.7 mm. (SWG22). Spread the primary evenly across the core, but leave some space at the centre for the two secondary turns that have to be wound subsequently.

When the board has been completed and checked thoroughly, a suitable mains transformer (9 V, 300 mA) or a 9 V mains adaptor may be connected to K<sub>3</sub>. Indicator D<sub>1</sub> should then light.

Using a multimeter, check whether a stable potential of 5 V exists across C<sub>32</sub> and C<sub>33</sub>. If so, it is virtually certain that the converter will work satisfactorily. If it does not, recheck the board thoroughly. It is not possible to give suitable test points, since all that can really be checked are the supply lines.

(960093-1)

6

 

**Figure 6. Mounting IC<sub>1</sub> may be a somewhat difficult task for beginners. Make sure that it is placed in the correct position.**