 


# simple copybit killer

*enables limitless digital copying*

The Serial Copy Management System (SCMS) prevents digital copying of audio material from the second generation onwards. Unfortunately, this protection also works on home recordings and so prevents home recordists from digitally copying their own

musical work more than once without degradation by the SCMS. This problem has been highlighted before in this magazine, but it has not gone away – reason enough to describe a simple and inexpensive circuit for permanently removing the copy-prohibit-bit from the S/PDIF\* audio signal.



## GENERAL DESCRIPTION

The circuit described in this article is intended for the digital recording or copying and playback of non-commercial musical work. Such recording or copying is possible only when the copy-prohibit has been eliminated without any other effect on the audio signal.

The design of the circuit is such that there are no modifications required in the existing audio installation. The circuit is simply inserted in series with the digital (optical or coaxial) link between the relevant recording and playback equipment.

Briefly, the circuit:

- requires no modification to the digital audio equipment;
- is suitable for use with signals on optical as well as coaxial lines;
- uses readily available components;
- operates without programmable ICs such as PALs and EPLDs;

- is easily set up;
- has good clock regeneration through the use of PLLs (jitterkiller);
- gives clear indication (LEDs) of the sampling frequency (32 kHz, 44.1 kHz, or 48 kHz);
- automatically recognizes, and switches over to, the correct sampling frequency;
- draws a small current owing to the use of CMOS ICs.

## CIRCUIT DESCRIPTION

The block diagram of the copybit killer is shown in **Figure 1**. It shows that the copybit killer consists of:

- optical-to-electrical converter for the S/PDIF signals;
- differentiating network;
- phase-locked loop (PLL) to regenerate the clock frequency;
- network for recognizing and processing the clock frequency;
- network for recognizing and dis-

Design by H. Hanft

\* Sony/Philips Digital Interface Format – the consumer version of the AES/EBU standard. This standard was devised by the American Audio Engineering Society and the European Broadcasting Union to define the signal format, electrical characteristics, and connectors, to be used for digital interfaces between professional audio products.

**WARNING.** The information contained in this article is intended solely for the recording, processing, and copying, of private musical work. The Editor and Publishers disclaim all responsibility for its use that infringes any copyright vested in commercial compact disks and (digital) tape cassettes. Such infringement is entirely the responsibility of the perpetrator.

**Figure 1. Block diagram of the copybit killer. The core of the circuit, 'decoding and disabling of the copy-prohibit-bit', uses an EPROM.**

- abling the copy-prohibit-bit;
- electrical-to-optical convertor for the S/PDIF signals.

The circuit diagram proper is shown in **Figure 2**. The operation of the various networks outlined above is described in the following sections.

The **optical-to-electrical conversion of the S/PDIF signal** is carried out by IC<sub>1</sub>, which is the well-known Type TORX173 integrated receiver. It converts the signal input from the fibre-glass cable into an electrical signal at TTL level. There is, of course, also a facility for inputting signals from a standard coaxial cable. This is possible via audio connector K<sub>1</sub> in parallel with the output of IC<sub>1</sub> via resistor R<sub>2</sub>.


The **differentiating circuit**, consisting of XOR gates IC<sub>2a</sub>-IC<sub>2c</sub> and RC networks R<sub>5</sub>-C<sub>3</sub> and R<sub>6</sub>-C<sub>4</sub>, serves to detect the rising or falling edges of the incoming S/PDIF signal. For each and every edge, a positive pulse of defined length is generated and used for synchronizing the following PLL.

The regeneration of the clock frequency contained in the S/PDIF signal is carried out by two discrete **phase-locked loops (PLLs)**. The first one is for frequencies 6.144 MHz (sampling rate 48 kHz) and 5.6448 MHz (sampling frequency 44.1 kHz), and the second for frequency 4.096 MHz (sampling frequency 32 kHz)

So as to keep the circuit simple, both PLLs are Type 74HCT4046 ICs (IC<sub>3</sub> and IC<sub>4</sub>). These circuits contain not only a phase comparator, but also a voltage-controlled oscillator (VCO). The PLLs circuits are virtually identical and differ only as far as the value of the resistor that sets the central frequency of the VCO is concerned (R<sub>7</sub> and R<sub>10</sub>).


The network for **recognizing the clock frequency** serves to detect the sampling frequency of the S/PDIF signal

**Figure 2. Circuit diagram of the copybit killer. All components are readily available and the circuit is easy to build and set up.**

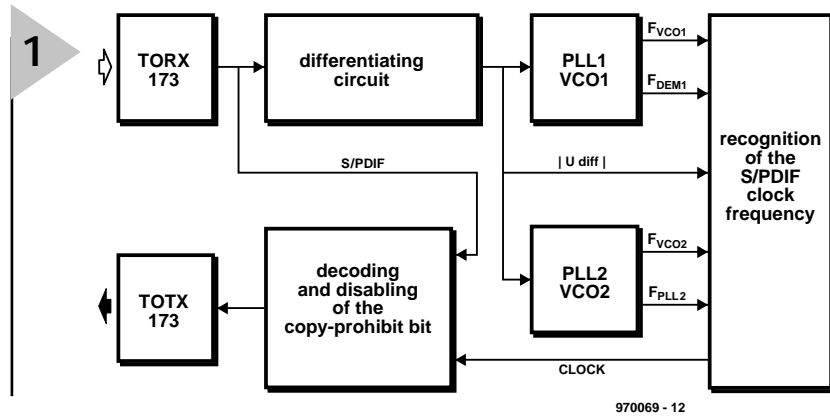

and pass this on to the decoder. It consists of IC<sub>5a</sub>-IC<sub>5d</sub> and four NOR gates, IC<sub>6a</sub>-IC<sub>6d</sub>. The comparators recognize the incoming S/PDIF signal and ensure

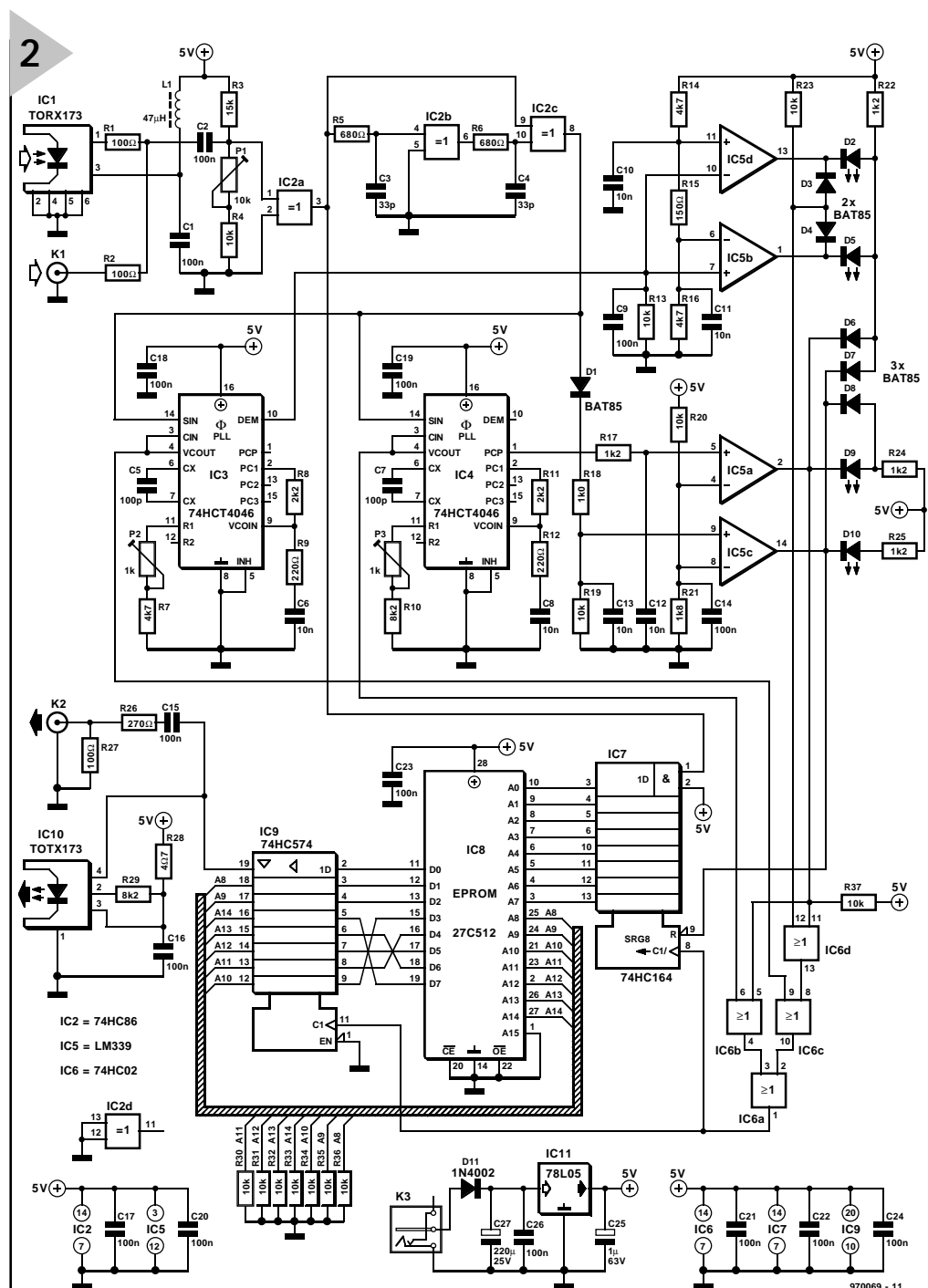that the PLL locked in at that moment is included in the signal processing. Also, when the sampling frequency is 48 kHz or 44.1 kHz, the VCO control



## Parts list

## Resistors:

$R_1, R_2, R_{27} = 100 \Omega$   
 $R_3 = 15 \text{ k}\Omega$   
 $R_4, R_{13}, R_{19}, R_{29}, R_{23},$   
 $R_{30}\text{--}R_{37} = 10 \text{ k}\Omega$   
 $R_5, R_6 = 680 \Omega$   
 $R_7, R_{14}, R_{16} = 4.7 \text{ k}\Omega$   
 $R_8, R_{11} = 2.2 \text{ k}\Omega$   
 $R_9, R_{12} = 220 \Omega$   
 $R_{10}, R_{29} = 8.2 \text{ k}\Omega$   
 $R_{15} = 150 \Omega$   
 $R_{17}, R_{22}, R_{24}, R_{25} = 1.2 \text{ k}\Omega$   
 $R_{18} = 1.0 \text{ k}\Omega$   
 $R_{21} = 1.8 \text{ k}\Omega$   
 $R_{26} = 270 \Omega$   
 $R_{28} = 4.7 \Omega$   
 $P_1 = 10 \text{ k}\Omega$  preset poten-  
 tiometer  
 $P_2, P_3 = 1 \text{ k}\Omega$  preset poten-  
 tiometer

## Capacitors:

$C_1, C_2, C_9, C_{14}\text{--}C_{24}, C_{26} =$   
 $0.1 \mu\text{F}$ , ceramic  
 $C_3, C_4 = 33 \text{ pF}$   
 $C_5, C_7 = 100 \text{ pF}$   
 $C_6, C_8, C_{10}\text{--}C_{13} = 0.01 \mu\text{F}$   
 $C_{25} = 1 \mu\text{F}$ , 63 V, radial  
 $C_{27} = 220 \mu\text{F}$ , 25 V, radial

## Inductors:

$L_1 = 47 \mu\text{H}$

## Semiconductors:

$D_1, D_3, D_4, D_6\text{--}D_8 = \text{BAT85}$   
 $D_2, D_5, D_9, D_{10} = \text{LED}$ , high  
 efficiency  
 $D_{11} = 1\text{N4002}$

## Integrated circuits:

$\text{IC}_1 = \text{TORX173}$   
 $\text{IC}_2 = 74\text{HC86}$   
 $\text{IC}_3, \text{IC}_4 = 74\text{HCT4046}$   
 $\text{IC}_5 = \text{LM339}$   
 $\text{IC}_6 = 74\text{HC02}$   
 $\text{IC}_7 = 74\text{HC164}$   
 $\text{IC}_8 = 27\text{C512}$  (available  
 ready programmed: Order  
 no 976516\* – see Readers  
 Services towards the end of  
 this issue)  
 $\text{IC}_9 = 74\text{HC574}$   
 $\text{IC}_{10} = \text{TOTX173}$   
 $\text{IC}_{11} = 78\text{L05}$

## Miscellaneous:

$K_1, K_2 = \text{audio socket for}$   
 PCB  
 $K_3 = \text{mains adaptor socket}$   
 for PCB  
 PCB Order no. 970069\* – see  
 Readers Services towards  
 the end of this issue

\* These items may be pur-  
 chased as a combination:  
 Order no. 970069-C


 
 
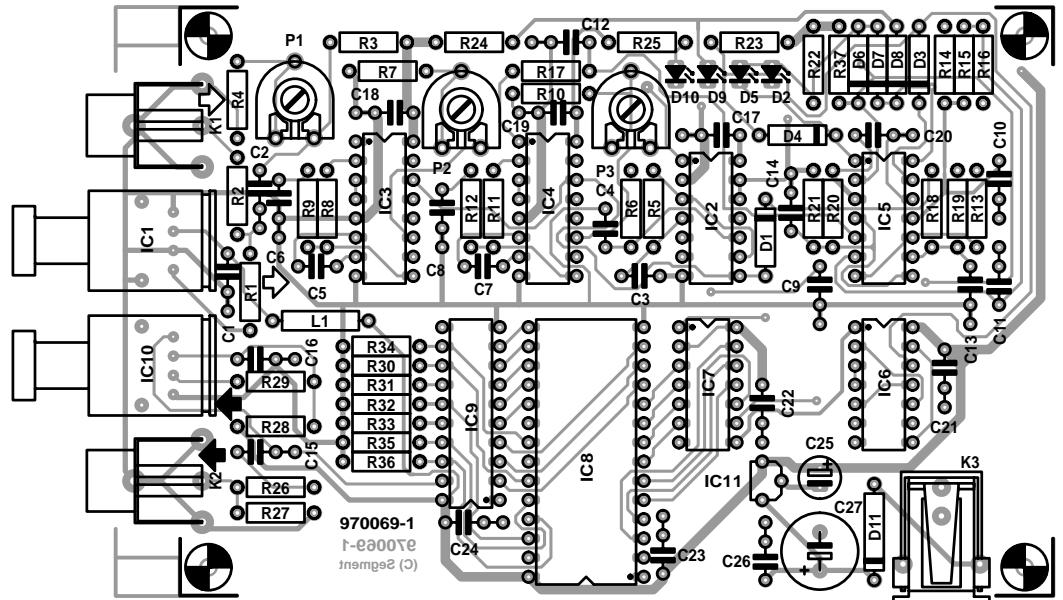


Figure 3. The printed-circuit board for the copybit killer is available ready-made.

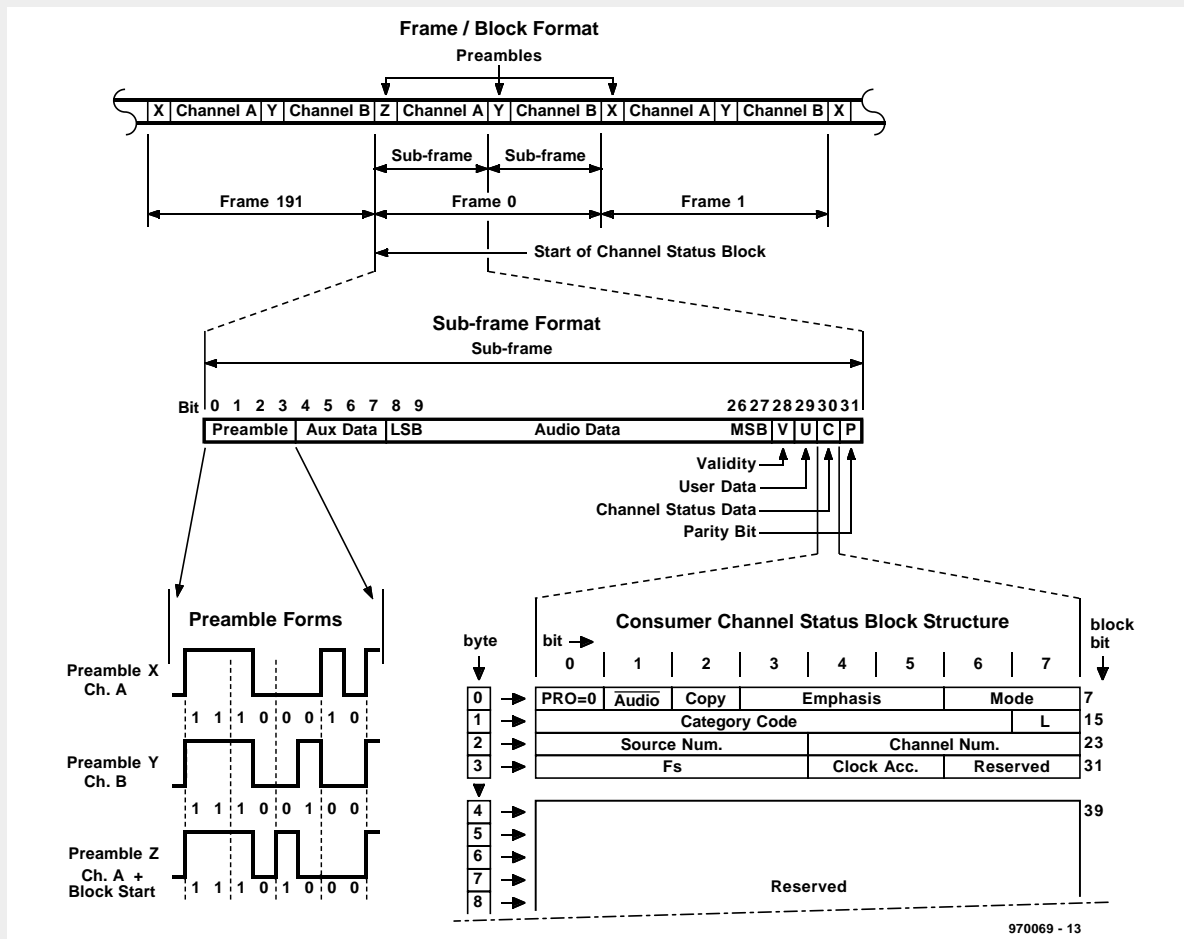

## Bit management

The digital part of the circuit, in conjunction with the associated programming code in the EPROM, provides a sequence control that recognizes and, if necessary, alters the status of the copy-prohibit-bit. The process attenuation of the S/PDIF signal is equal to one clock cycle. Shift register IC<sub>7</sub> continuously separates the last eight biphasic-bit halves from the serial data stream and arranges that the halves are available at A<sub>0</sub>-A<sub>7</sub>.

The feedback of the data lines to the address lines via latch IC<sub>9</sub> divides the memory of the EPROM into 128 blocks of 256 bytes each. In this way it becomes possible within a block, depending on the status of address lines A<sub>0</sub>-A<sub>7</sub>, to select the same or another block which is then enabled at the rising edge of the next clock pulse. This arrangement provides processing control in up to 128 steps.

From the format of the S/PDIF signal in the diagram above, it is seen that a transfer block consists of 192 frames, each of which is composed of two sub-frames. These sub-frames start with a preamble (X, Y, Z) and contain 32 bits. The preambles serve to mark the onset of a sub-frame; preamble Z also indicates the start of a new transfer block.

Bit 2 of the Consumer Channel Status Block is of special importance for the present copybit killer, because unlimited digital copying can be carried out only when this bit is set. The Channel Status Bit is located at bit position 30 (biphase-bit-half positions 60 and 61) of a sub-frame and therefore occurs twice during each frame.

As far as the copy-prohibit-bit is concerned, these are the sub-frames of frame number 2.

In short, it is necessary that the status of bit number 30 in the two sub-frames of frame 2 be recognized and, if this bit has been erased, that it is set. If one of these bits is altered, the next parity bit (bit position 31) of the sub-frame must be inverted. This may give rise to eight different situations, which have to be taken into account in the programming code in the EPROM—see Table.

Bit Bi-Bit	User Data		Channel Status Data		Parity Bit		
	29	58	59	60	61	30	31
Case 1	*	*	*	0	0	1	0
C=0, P=1	↓	↓	↓	↓	↓	↓	↓
Case 2	*	*	*	0	1	0	1
C=0, P=0	↓	↓	↓	↓	↓	↓	↓
Case 3	*	*	*	0	1	0	0
C=1, P=0	↓	↓	↓	↓	↓	↓	↓
Case 4	*	*	*	0	1	0	1
C=1, P=1	↓	↓	↓	↓	↓	↓	↓
Case 5	*	*	*	1	0	1	0
C=1, P=1	↓	↓	↓	↓	↓	↓	↓
Case 6	*	*	*	1	0	1	1
C=1, P=0	↓	↓	↓	↓	↓	↓	↓
Case 7	*	*	*	1	1	0	0
C=0, P=0	↓	↓	↓	↓	↓	↓	↓
Case 8	*	*	*	1	1	0	1
C=0, P=1	↓	↓	↓	↓	↓	↓	↓

